

---


## Electronics for FNAL mini-TPC

---


Dan Edmunds work  
reported by Carl Bromberg

# Hybrid preamplifier

D-zero Run-II

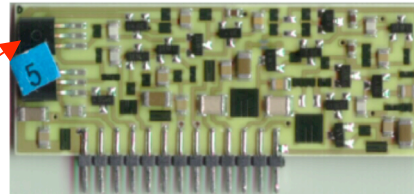


Dual FET  
input stage

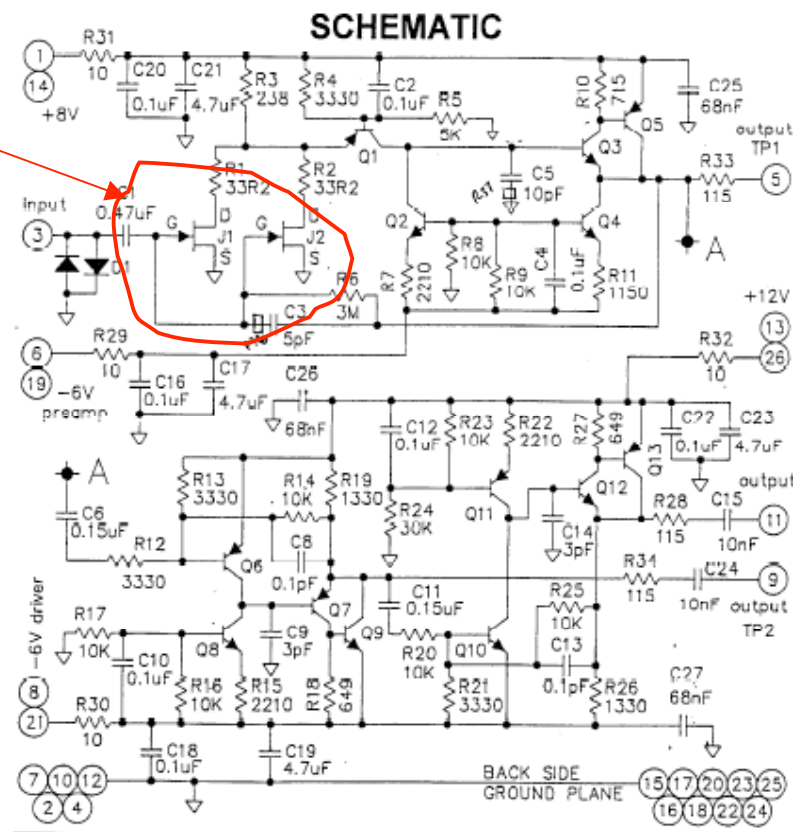

Output


# Analog to digital conversion

D-zero Run-II  
ADF-2 card

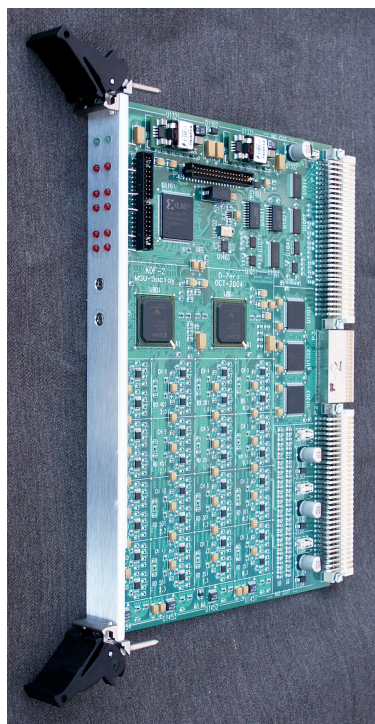


FPGA data storage  
field programmable

Example: 2048  
samples @ 197 ns

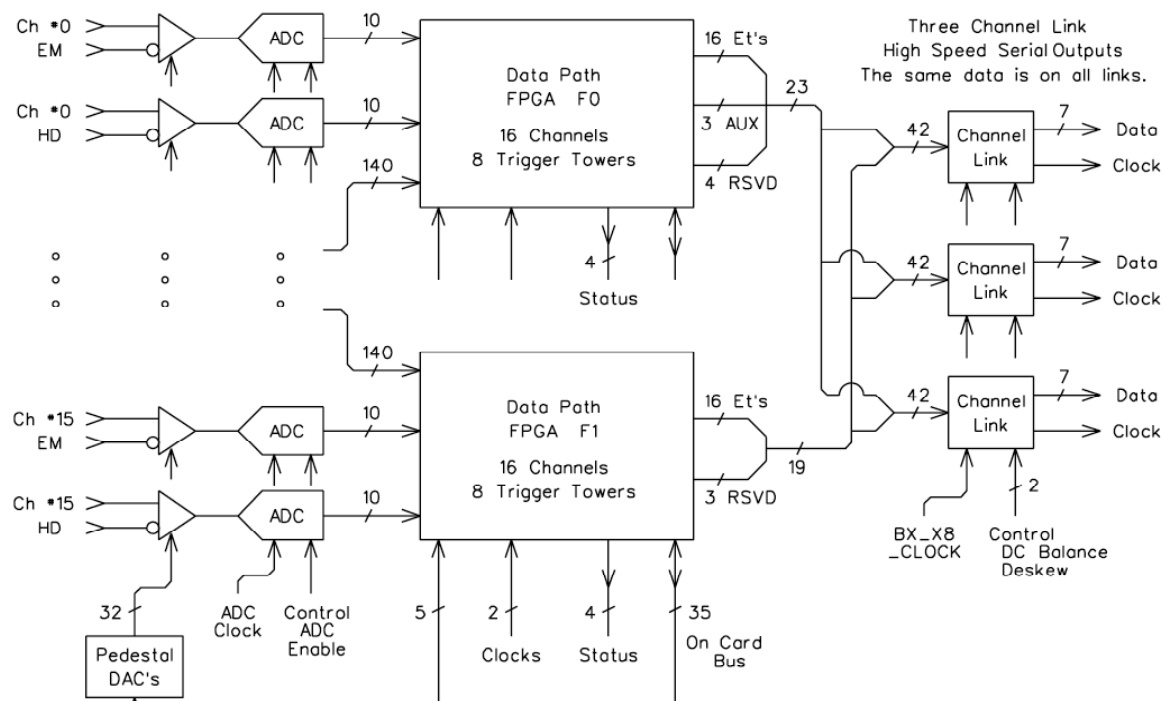

# Test setup


---

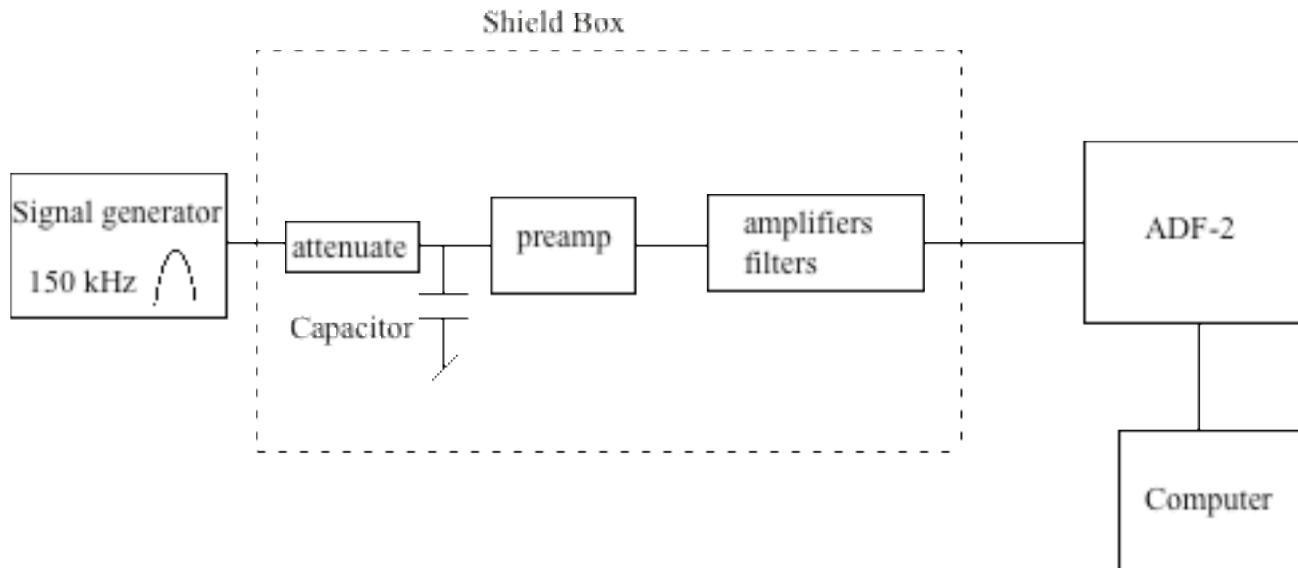




# 22,000 electron signal

Capacitance 0-pf

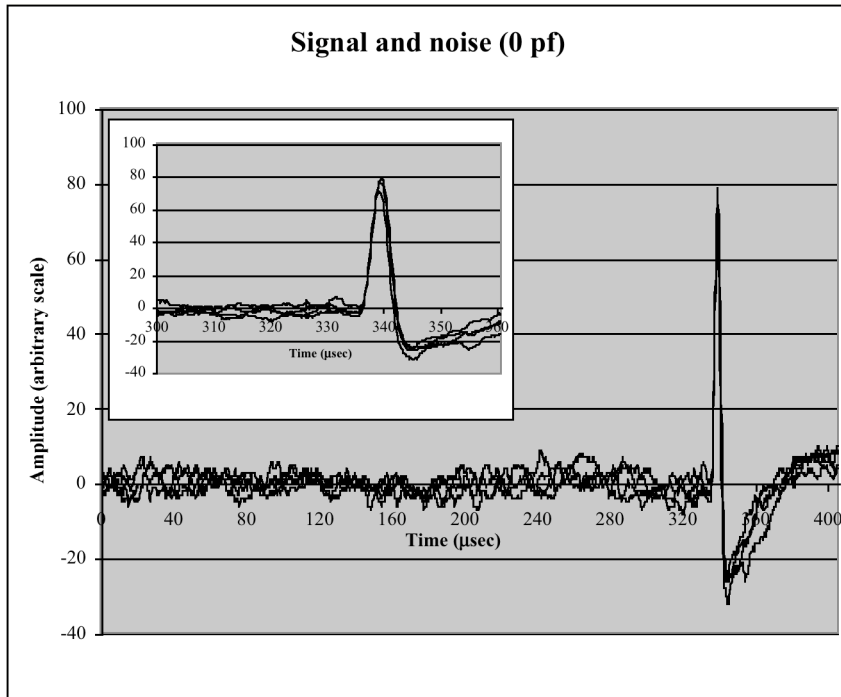


Capacitance 600-pf

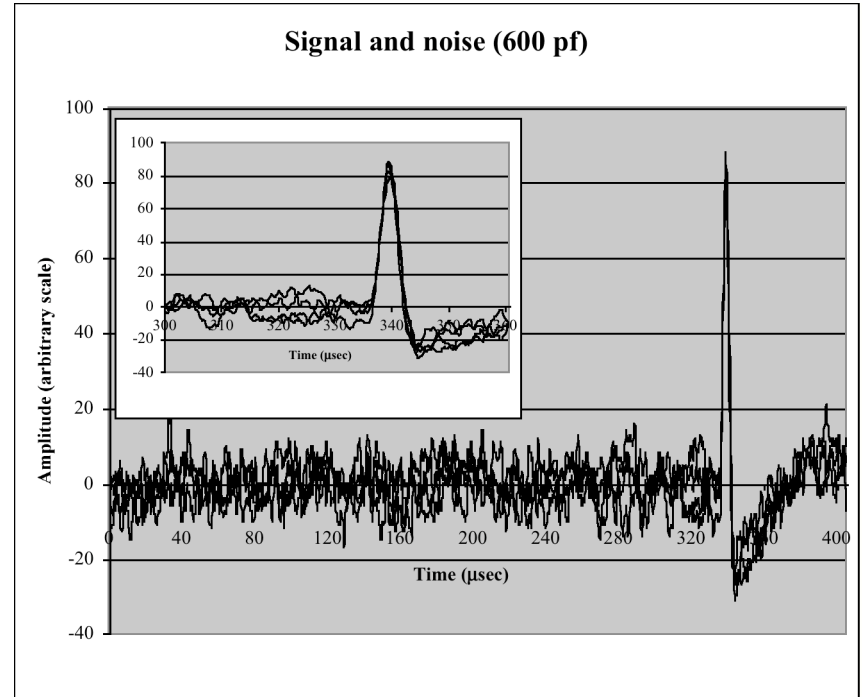

# Noise spectrum

High pass & low pass filtered

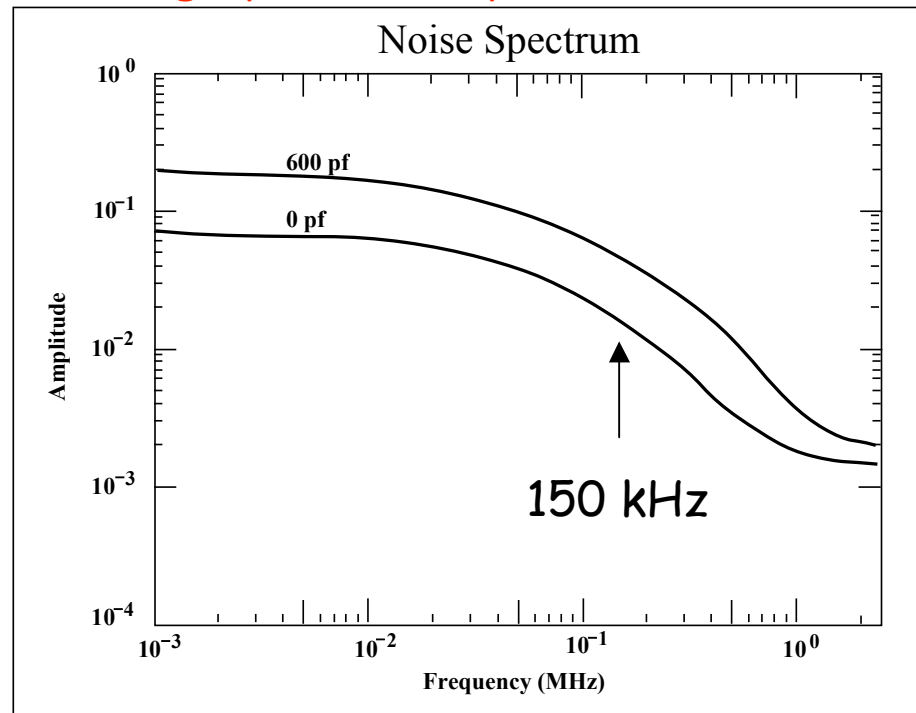


# Wire signals

No cross talk on neighboring wires.


SS Wire resistance  $\sim 100$  Ohms/m

Capacitance  $\sim 6$  pf/m

Dispersion of signal from far end.

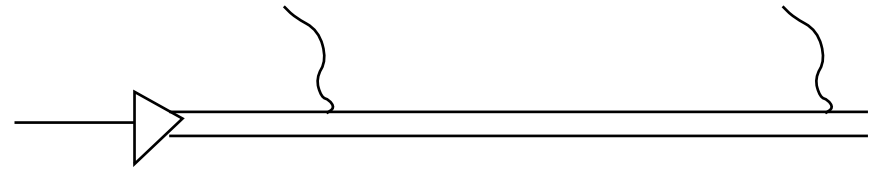

## Johnson Noise

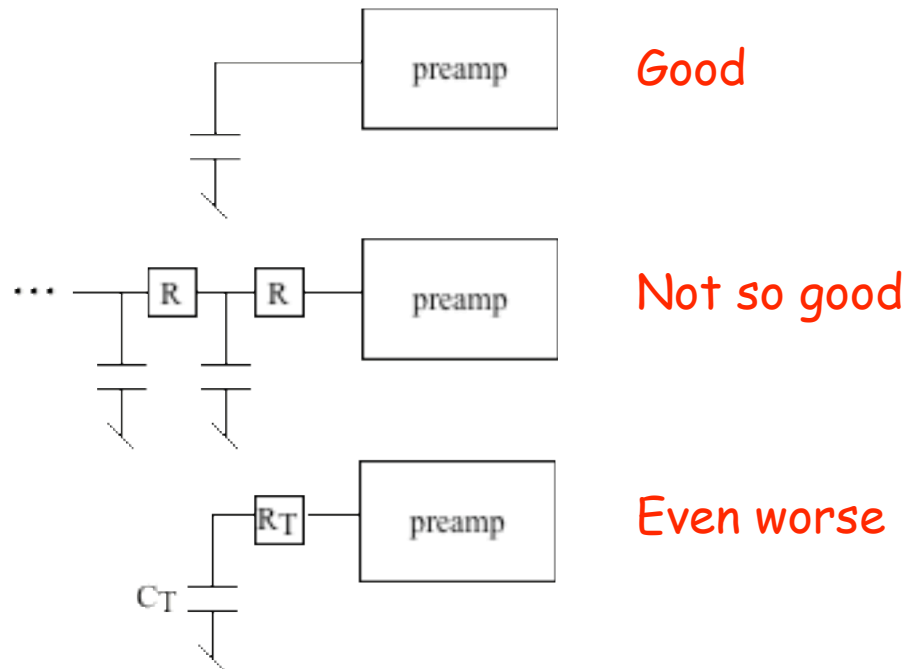

## ICARUS

SS wires. Why?

CuBe wires  $\sim 5$  Ohms/m